



5: Register File

5.1 register4.vhd

```
--MIPS Part_5
--Register 4bit
--27/05/2020, Konstantinos Gkousaris, 711171073, UniWA--
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```

```
ENTITY register4 IS PORT (
d : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
resetn, clk : IN STD_LOGIC;
q : OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
END register4;
```

```
ARCHITECTURE behavioral OF register4 IS
BEGIN
    PROCESS(resetn, clk)
    BEGIN
        IF resetn = '0' THEN
            q <= "0000";
        ELSIF rising_edge(clk) THEN
            q <= d;
        END IF;
    END PROCESS;
END behavioral;
```

5.1 register4 testbench.vhd

```
--test bench code
--runs for 800ns
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```

```
ENTITY test_register4 IS
END test_register4;
```


```
ARCHITECTURE behavioral OF test_register4 IS
    COMPONENT register4 PORT(
        d : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        resetn, clk : IN STD_LOGIC;
        q : OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
    END COMPONENT;
```

```

signal reset1 : STD_LOGIC:='1';
signal clk1 : STD_LOGIC;
signal d1 : STD_LOGIC_VECTOR(3 DOWNT0 0);
signal q1 : STD_LOGIC_VECTOR(3 DOWNT0 0);
constant clk_period : time := 100 ns;

BEGIN
REG4 : register4 PORT MAP (
    d => d1,
    q => q1,
    resetn => reset1,
    clk => clk1);
--process for clock
clk_process :PROCESS
BEGIN
    clk1 <= '0';
    wait for clk_period/2;
    clk1 <= '1';
    wait for clk_period/2;
END PROCESS;
--process which controls the 'd' entry
simulation : PROCESS
BEGIN
    d1 <= "0010"; wait for 200 ns; --different entries every 200 ns
    d1 <= "1110"; wait for 200 ns;
    d1 <= "1010"; wait for 200 ns;
END PROCESS;
END;

```

 

Πίνακας Λειτουργίας

In	Out
0010	0010
1110	1110
1010	1010

5.2 registerfile.vhd

```
--MIPS Part_5
--RegisterFile
--27/05/2020, Konstantinos Gkousaris, 711171073, UniWA--
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;

ENTITY registerfile IS PORT (
    Datin : IN STD_LOGIC_VECTOR(3 downto 0);
    Addr  : IN STD_LOGIC_VECTOR(2 downto 0);
    we    : IN STD_LOGIC;
    clk   : IN STD_LOGIC;
    Dataout : OUT STD_LOGIC_VECTOR(3 downto 0));
END registerfile;

ARCHITECTURE behavioral OF registerfile IS

TYPE regArray IS ARRAY(0 TO 7) OF STD_LOGIC_VECTOR(3 DOWNTO 0);

    SIGNAL registerfile: regArray;
BEGIN
    PROCESS(clk)
    BEGIN
        IF (clk'event and clk='0') THEN
            IF we='1' THEN
                registerfile(to_integer(unsigned(Addr))) <= Datin;
            END IF;
        END IF;
        Dataout <= registerfile(to_integer(unsigned(Addr)));
    END PROCESS;
END;
```

5.2 registerfile_testbench.vhd

```
--test bench code
--this test bench runs for 800 ns
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;

ENTITY test_registerfileMP IS
END test_registerfileMP;

ARCHITECTURE behavioral OF test_registerfileMP IS

    COMPONENT registerfile PORT(
        Datin : IN STD_LOGIC_VECTOR(3 downto 0);
        Addr  : IN STD_LOGIC_VECTOR(2 downto 0);
        we    : IN STD_LOGIC;
        clk   : IN STD_LOGIC;
        Dataout : OUT STD_LOGIC_VECTOR(3 downto 0));
    END COMPONENT;
```

```

--component signals
signal Datain1,Dataout1 : std_logic_vector(3 downto 0);
signal Addr1 : std_logic_vector(2 downto 0);
signal we1,clk1 : std_logic;

constant clk_period : time := 100 ns;


BEGIN
    REGISTERFILE1 : registerfile PORT MAP (
        Datain=>Datain1,
        Addr=>Addr1,
        we=>we1,
        clk=>clk1,
        Dataout=>Dataout1);
    --process for clock
    clk_process :PROCESS
    BEGIN
        clk1 <= '0';
        wait for clk_period/2;
        clk1 <= '1';
        wait for clk_period/2;
    END PROCESS;

    write_process : PROCESS
    BEGIN
        we1 <= '1'; wait for 400 ns;  --write for 400 ns
        we1 <= '0'; wait for 400 ns;  --read for 400 ns
    END PROCESS;

    simulation : PROCESS
    BEGIN
        -- write this data in memory
        Datain1 <= "0101"; wait for 100 ns;
        Datain1 <= "1101"; wait for 100 ns;
        Datain1 <= "0010"; wait for 100 ns;
        Datain1 <= "1001"; wait for 100 ns;
        --after specific inputs reset the datain
        Datain1 <= "0000"; wait;
    END PROCESS;

    address_process : PROCESS
    BEGIN
        --write the data on a specific address for 400ns
        addr1 <= "000"; wait for 100 ns;
        addr1 <= "001"; wait for 100 ns;
        addr1 <= "010"; wait for 100 ns;
        addr1 <= "011"; wait for 100 ns;
        --read the data from memory to check if writing process works good
        addr1 <= "000"; wait for 100 ns;
        addr1 <= "001"; wait for 100 ns;
        addr1 <= "010"; wait for 100 ns;
        addr1 <= "011"; wait for 100 ns;
    END PROCESS;
END;

```

 

Πίνακας Λειτουργίας

Διεύθυνση	Λειτουργία(we)	Περιεχόμενα(DataIN)
000	1 (write)	0101
001	1 (write)	1101
010	1 (write)	0010
011	1 (write)	1001
000	0 (read)	0101
001	0 (read)	1101
010	0 (read)	0010
011	0 (read)	1001

5.3 registerfile_full.vhd

```
--MIPS Part_5
--RegisterFileFull
--27/05/2020, Konstantinos Gkousaris, 711171073, UniWA--
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;
```

```
ENTITY registerfile_full IS
    GENERIC (
        dw : natural := 4;
        size : natural := 4;
        adrw : natural := 2);
```

```

PORT (      Datain : IN STD_LOGIC_VECTOR(dw-1 downto 0);
          rAddr1: IN STD_LOGIC_VECTOR(adrw-1 downto 0);
          rAddr2: IN STD_LOGIC_VECTOR(adrw-1 downto 0);
          wAddr : IN STD_LOGIC_VECTOR(adrw-1 downto 0);
          we : IN STD_LOGIC;
          clk : IN STD_LOGIC;
          reset : IN STD_LOGIC;
          Dataout1 : OUT STD_LOGIC_VECTOR(dw-1 downto 0);
          Dataout2 : OUT STD_LOGIC_VECTOR(dw-1 downto 0));

end registerfile_full;

ARCHITECTURE behavioral OF registerfile_full IS

TYPE regArray IS ARRAY(0 to size-1) OF std_logic_vector(dw-1 DOWNTO 0);
signal regfileb : regArray;

BEGIN
    PROCESS(clk)
    BEGIN
        IF reset= '1' THEN --reset entire circuit
            Dataout1 <= "0000" ;
            Dataout2 <= "0000" ;
        ELSIF (clk'event AND clk='0') then
            IF we='1' then
                regfileb(to_integer(unsigned(wAddr))) <= Datain;
            END IF;
        END IF;
        Dataout1 <= regfileb(to_integer(unsigned(rAddr1)));
        Dataout2 <= regfileb(to_integer(unsigned(rAddr2)));
    END PROCESS;
END behavioral;

```

5.3 registerfile full testbench.vhd

```

--test bench code
--this test bench runs for 1200ns
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;

ENTITY test_registerfilefull IS
END test_registerfilefull;

ARCHITECTURE behavioral OF test_registerfilefull IS

    --variables for generic to pass into component
    signal dw : natural := 4;
    signal size : natural := 4;
    signal adrw : natural := 2;

    COMPONENT registerfile_full PORT(
        Datain : IN STD_LOGIC_VECTOR(dw-1 downto 0);
        rAddr1: IN STD_LOGIC_VECTOR(adrw-1 downto 0);
        rAddr2: IN STD_LOGIC_VECTOR(adrw-1 downto 0);
        wAddr : IN STD_LOGIC_VECTOR(adrw-1 downto 0);
        we : IN STD_LOGIC;
        clk : IN STD_LOGIC;
        reset : IN STD_LOGIC;
        Dataout1 : OUT STD_LOGIC_VECTOR(dw-1 downto 0);
        Dataout2 : OUT STD_LOGIC_VECTOR(dw-1 downto 0));
    END COMPONENT;

```

```

--component signals
signal A1,C1,B1 : std_logic_vector(4-1 downto 0);--dw
signal rAddr1a, rAddr2b, wAddr1 : std_logic_vector(2-1 downto 0);--adrw
signal we1,clk1, reset1 : std_logic;
constant clk_period : time := 200 ns;
BEGIN --this test bench runs for 1200ns
    REGISTERFILE_FULL1 : registerfile_full PORT MAP (
        Datain => a1,
        rAddr1 => rAddr1a,
        rAddr2 => rAddr2b,
        wAddr => wAddr1,
        we => we1,
        reset => reset1,
        clk => clk1,
        Dataout1 => c1,
        Dataout2 => b1);
--process for clock

    clk_process :PROCESS
    BEGIN
        clk1 <= '0';
        wait for clk_period/2;
        clk1 <= '1';
        wait for clk_period/2;
    END PROCESS;

    write_process : PROCESS
    BEGIN
        we1 <= '1'; wait for 800 ns;  --write for 800 ns
        we1 <= '0'; wait for 400 ns;  --read for 400 ns
    END PROCESS;

    simulation : PROCESS
    BEGIN
        a1 <= "0101"; wait for 200 ns;  --different entries every 200ns
        a1 <= "1101"; wait for 200 ns;
        a1 <= "0010"; wait for 200 ns;
        a1 <= "1001"; wait for 200 ns;
    END PROCESS;

    write_address_process : PROCESS
    BEGIN
        wAddr1 <= "00"; wait for 200 ns; --change address every 200ns
        wAddr1 <= "01"; wait for 200 ns;
        wAddr1 <= "10"; wait for 200 ns;
        wAddr1 <= "11"; wait for 200 ns;
    END PROCESS;

    read1_address_process : PROCESS
    BEGIN
        wait for 800 ns;
        rAddr1a <= "00"; wait for 200 ns;
        rAddr1a <= "10"; wait for 200 ns;
    END PROCESS;

    read2_address_process : PROCESS
    BEGIN
        wait for 800 ns;
        rAddr2b <= "01"; wait for 200 ns;
        rAddr2b <= "10"; wait for 200 ns;
    END PROCESS;

```

```
reset_prosess : PROCESS
BEGIN
    reset1 <= '0'; wait for 1200 ns;
END PROCESS;
```

END;



Πίνακας Λειτουργίας

Λειτουργία	Διευθυνσή	WR	DR1	DR2
write	00	0101	xxxx	xxxx
write	01	1101	xxxx	xxxx
write	10	0010	xxxx	xxxx
write	11	1001	xxxx	xxxx
read	00 & 10	0101	0101	0010
read	01 & 10	1101	1101	0010